

$$V = IR$$

$$V_{\infty} = I_{\infty} \cdot 1.923$$

$$\frac{R}{L} = 1.923$$

$$\approx 2$$

$$s = 2$$

$$P = 13$$

$$b \in 4$$

$$s^2 + 4s + 43$$

$$\frac{(s+2)(s-2)^2}{((s+2)^2 + 9)(s-2)^2}$$

$$(s-2)(s+2)(s-2)(s+2)$$

$$\frac{(s-2)^2(s+2)^2 + 9(s-2)^2}{(s-2)(s+2)(s-2)(s+2) + 9(s-2)^2}$$

$$y \rightarrow I_s$$

$$x \rightarrow V_s$$

$$T_s = \frac{I_s}{V_s}$$

$$I_s = V_s \cdot I_s$$

$$y = mx + c$$

$$y =$$

$$\frac{100}{s+1}$$

$$(5 \text{ marks}) \frac{0.1}{0.01s+1}$$

$$(5)$$

$$(5)$$

$$Z = \begin{bmatrix} 10 & 5 \\ 5 & 9 \end{bmatrix}$$

$$V_0 = 5V$$

$$(7)$$

$$(8 \text{ marks})$$

EMT 3105: CIRCUIT AND NETWORK THEORY II CAT I

19 JUNE 2025

TIME 1:00PM

1 HOUR

ANSWER ALL QUESTIONS

- a) For the transfer function given, sketch the bode diagram which shows how the phase of the system is affected by changing input frequency

$$TF = \frac{1}{2s + 100}$$

- b) Find Laplace inverse transform of (marks)

$$\frac{\frac{s+2}{(s+2)^2+9}}{s+2} - \frac{s+a}{(s+a)^2+\omega^2}$$

- c) Determine the y parameters for a two-port network if the z parameters are (marks)

- d) Find $v(t)$ for $t > 0$, $v(0) = 5V$, $i(0) = 0$. Consider three cases in Fig 3(a):

- i. Case one $R = 1.923 \Omega$

(marks)

- ii. Case two $R = 5 \Omega$